

Practical 8

AIM: To implement Full Subtractor and Half Subtractor in Logisim Simulator

- HALF SUBTRACTOR**

Inputs		Outputs	
A	B	Diff	Borrow
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0


$$\text{Diff} = A'B + AB'$$

$$\text{Diff} = A \oplus B$$

AND,

$$\text{Borrow} = A'B$$

Implementation:

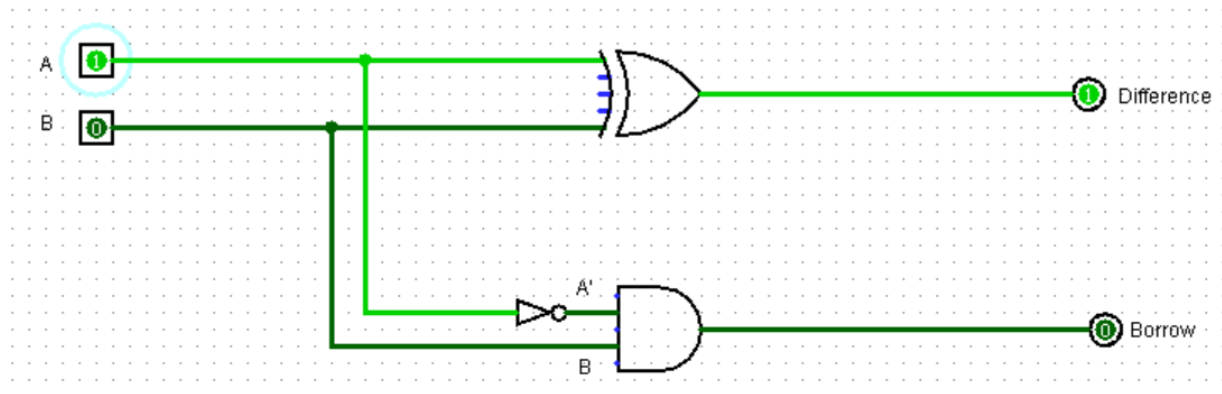

- FULL SUBTRACTOR**

Inputs			Outputs	
A	B	Borrow _{in}	Diff	Borrow
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1


For Difference :

A \ B Bin	00		01		11		10	
	0		1		3		2	
0	0		1		3		2	
1	4		5		7		6	

For Borrow :

A \ B Bin	00		01		11		10	
	0		1		3		2	
0	0		1		3		2	
1	4		5		7		6	

Implementation:

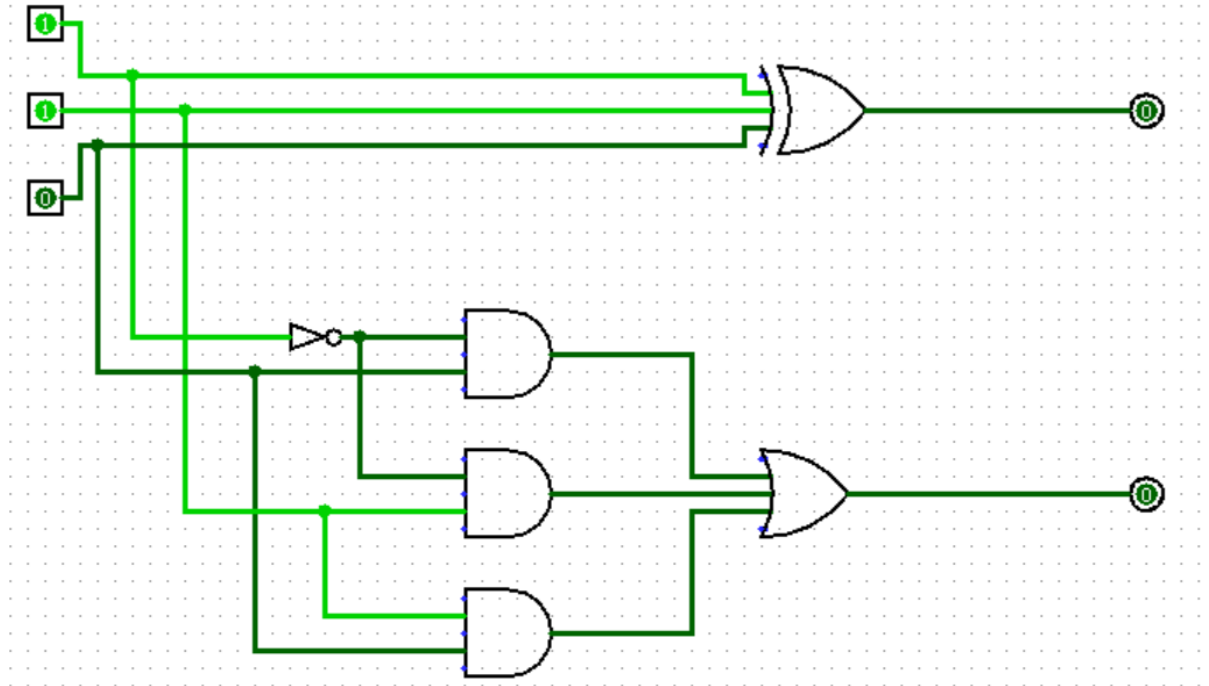

Rubric wise marks obtained:


Rubrics	Regularity		Problem Understanding & Implementation of Solution in Simulator		Testing of the Solution		Documentation		Mock Viva Test		Total out of 10
	Good (2)	Avg. (1)	Good (2)	Avg. (1)	Good (2)	Avg. (1)	Good (2)	Avg. (1)	Good (2)	Avg. (1)	

Faculty Signature


Practical 9

AIM: To implement four bit by three-bit binary multiplier

Theory:

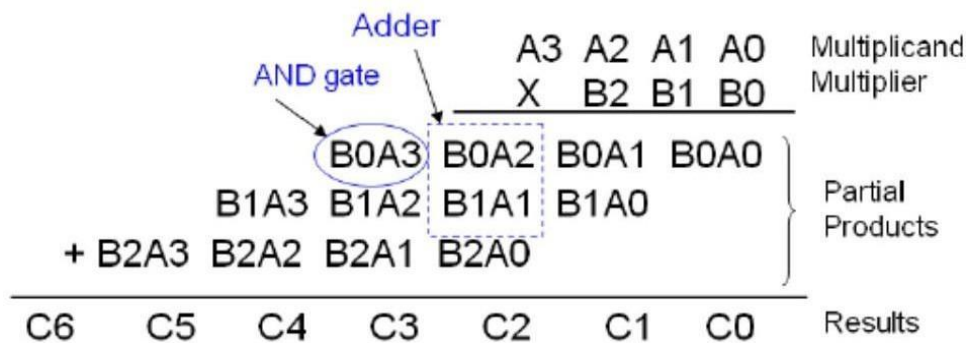

Implementation:

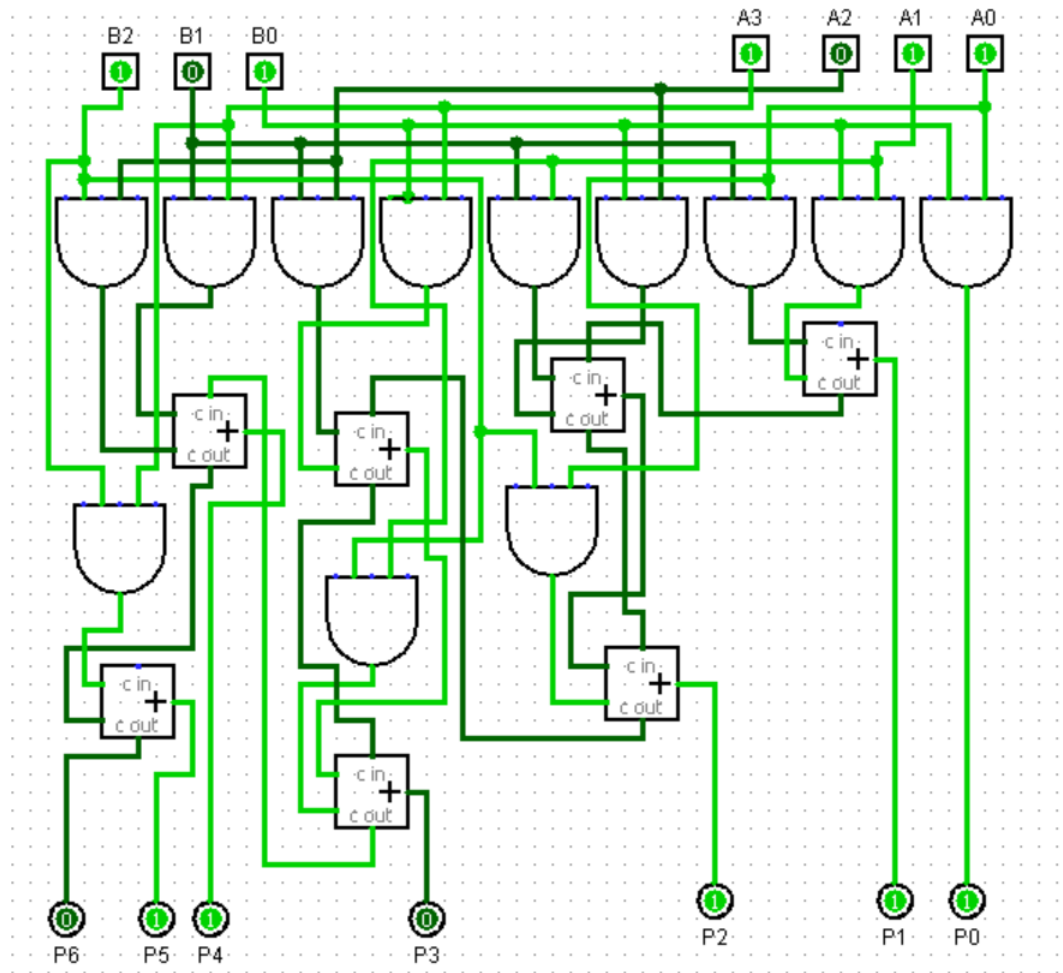

Rubric wise marks obtained:

Rubrics	Regularity		Problem Understanding & Implementation of Solution in Simulator		Testing of the Solution		Documentation		Mock Viva Test		Total out of 10
	Good (2)	Avg. (1)	Good (2)	Avg. (1)	Good (2)	Avg. (1)	Good (2)	Avg. (1)	Good (2)	Avg. (1)	

Faculty Signature


Enrolment No: - 230170116023

Page No 36


Practical 10

AIM: To implement BCD adder in Logisim simulator

Theory:

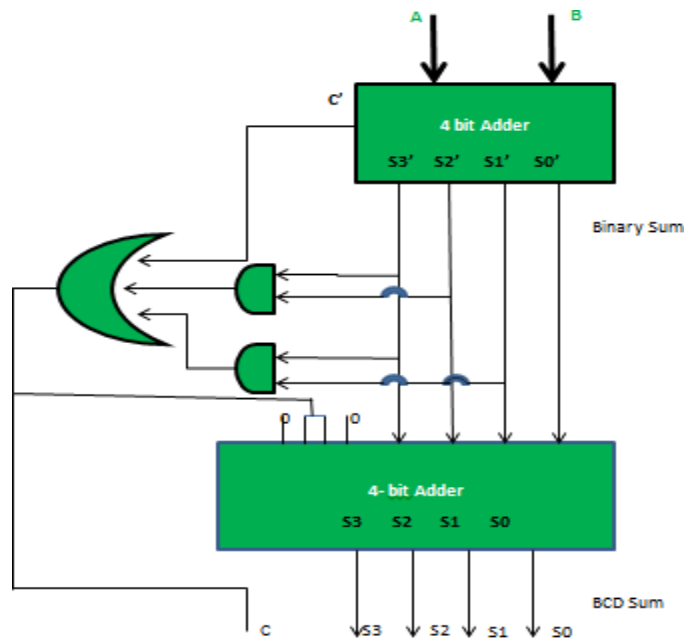

Implementation:

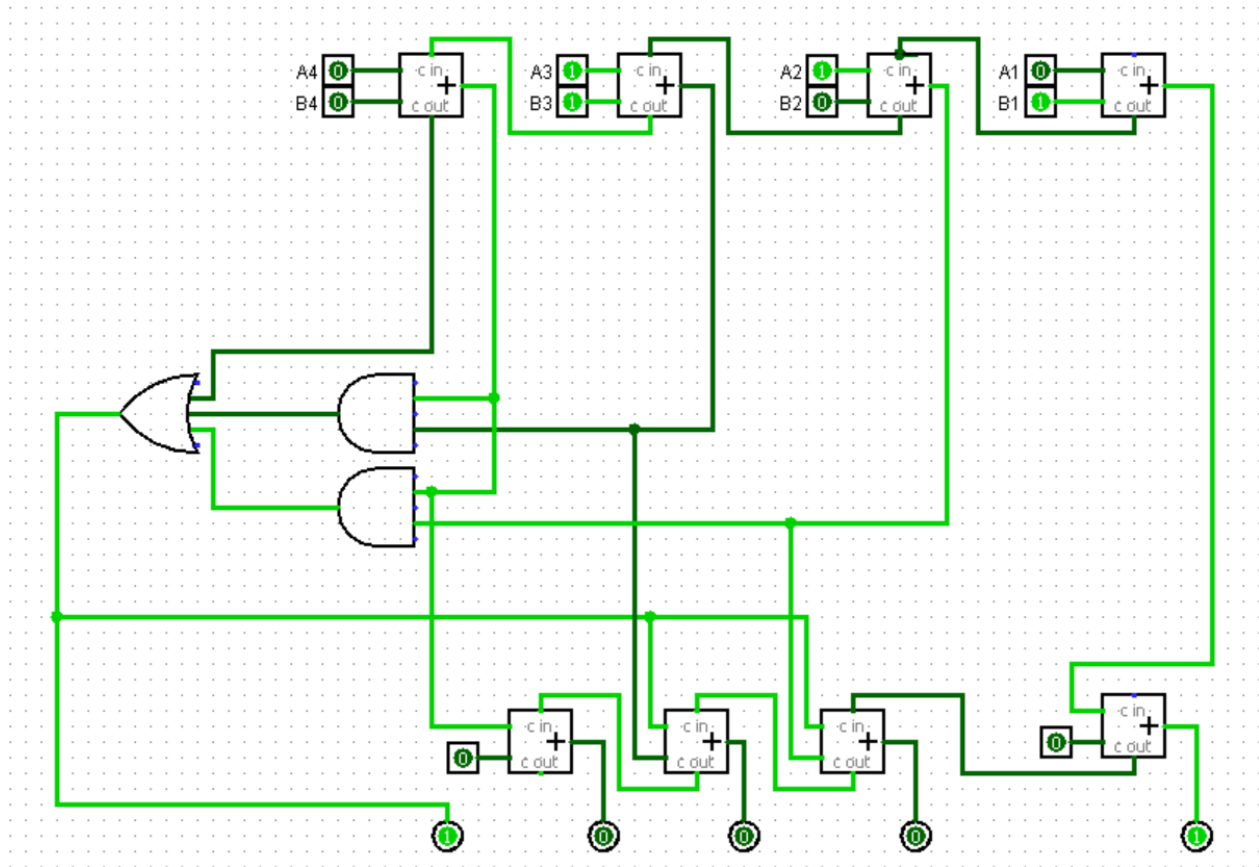

Rubric wise marks obtained:

Rubrics	Regularity		Problem Understanding & Implementation of Solution in Simulator		Testing of the Solution		Documentation		Mock Viva Test		Total out of 10
	Good (2)	Avg. (1)	Good (2)	Avg. (1)	Good (2)	Avg. (1)	Good (2)	Avg. (1)	Good (2)	Avg. (1)	

Faculty Signature

Practical 11

AIM: To implement Magnitude Comparator in Logisim Simulator

Theory:


Inputs				Outputs		
A ₁	A ₀	B ₁	B ₀	A>B	A=B	A<B
0	0	0	0	0	1	0
0	0	0	1	0	0	1
0	0	1	0	0	0	1
0	0	1	1	0	0	1
0	1	0	0	1	0	0
0	1	0	1	0	1	0
0	1	1	0	0	0	1
0	1	1	1	0	0	1
1	0	0	0	1	0	0
1	0	0	1	1	0	0
1	0	1	0	0	1	0
1	0	1	1	0	0	1
1	1	0	0	1	0	0
1	1	0	1	1	0	0
1	1	1	0	1	0	0
1	1	1	1	0	1	0

FOR A>B :

A ₁ A ₀ \ B ₁ B ₀				
	00	01	11	10
00	0	1	3	2
01	4	5	7	6
11	12	13	15	14
10	8	9	11	10

$$A > B = A_1' B_1' + A_0 B_1' B_0' + A_1 A_0 B_0'$$

Implementation:

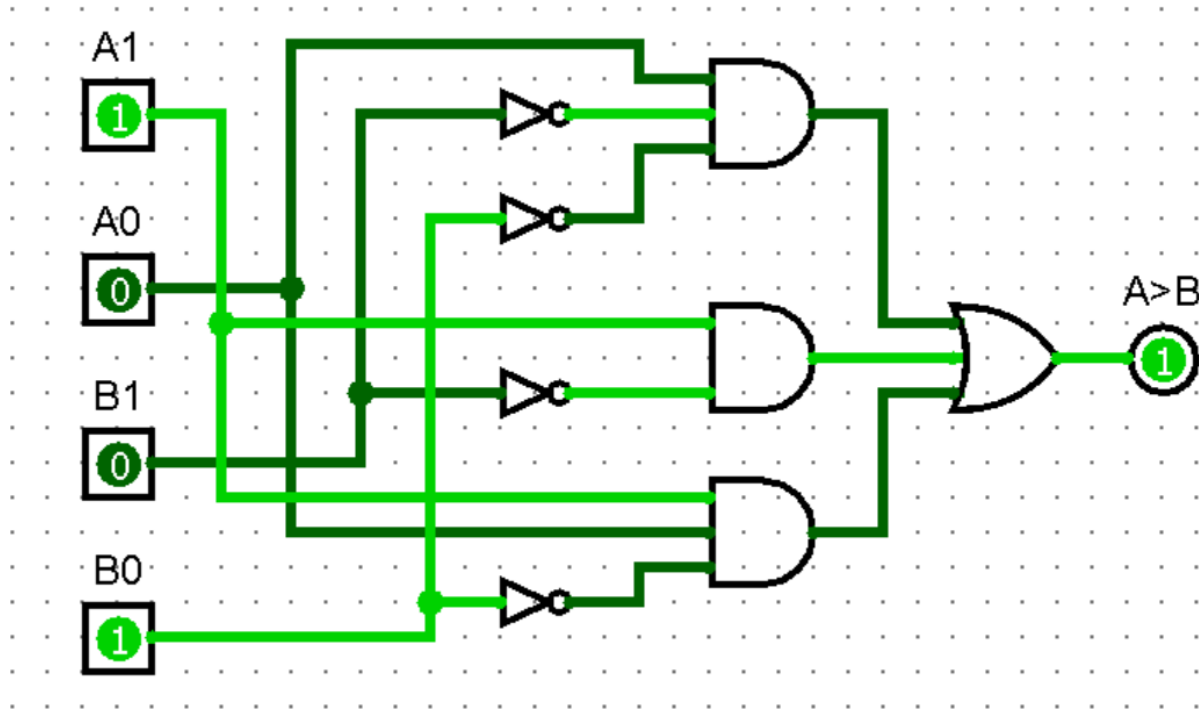


FOR A = B :

B1B0 \ A1A0	00	01	11	10
00	0	1	3	2
01	4	5	7	6
11	12	13	15	14
10	8	9	11	10

$$\{A = B\} = A_1' A_0' B_1' B_0' + A_1' A_0 B_1' B_0 + A_1 A_0' B_1 B_0' + A_1 A_0 B_1 B_0$$

Implementation:

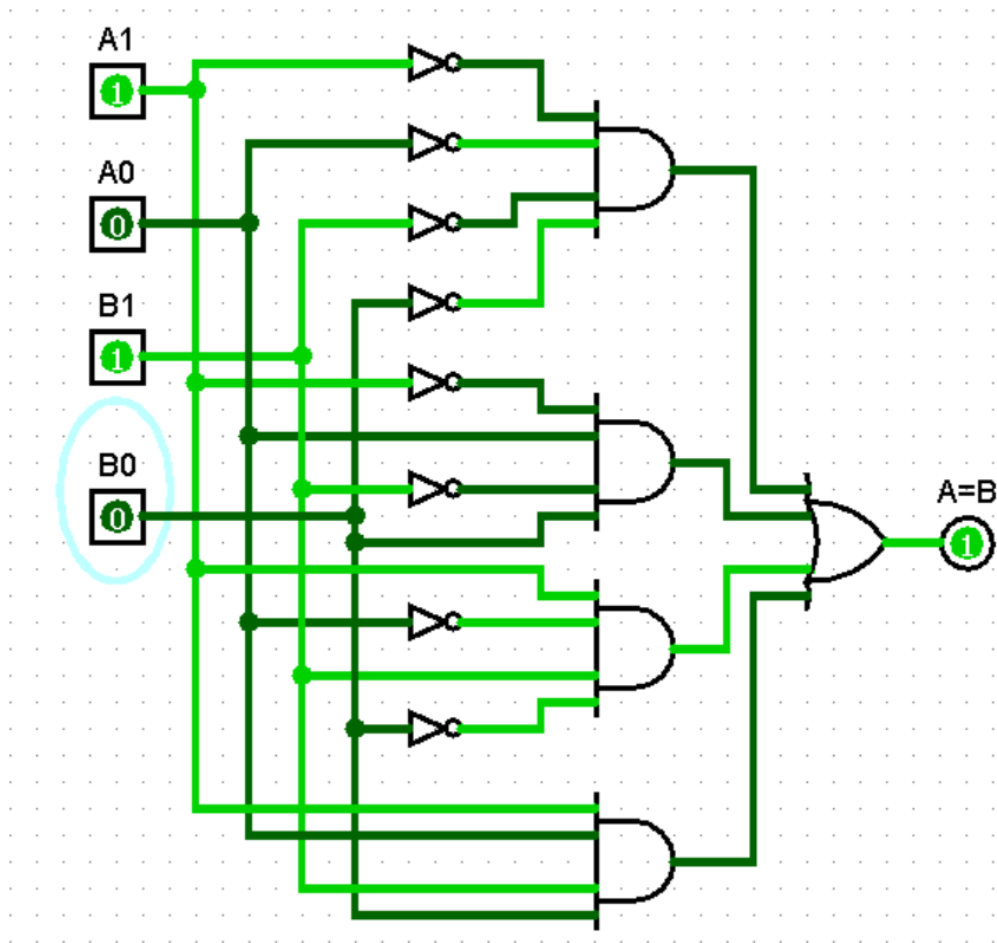


For $A < B$:

A1A0 \ B1B0	B1B0			
	00	01	11	10
00	0	1	3	2
01	4	5	7	6
11	12	13	15	14
10	8	9	11	10

$$\{ A < B \} = A_1' B_1 + A_1' A_0' B_0 + A_0' B_1 B_0$$

Implementation:

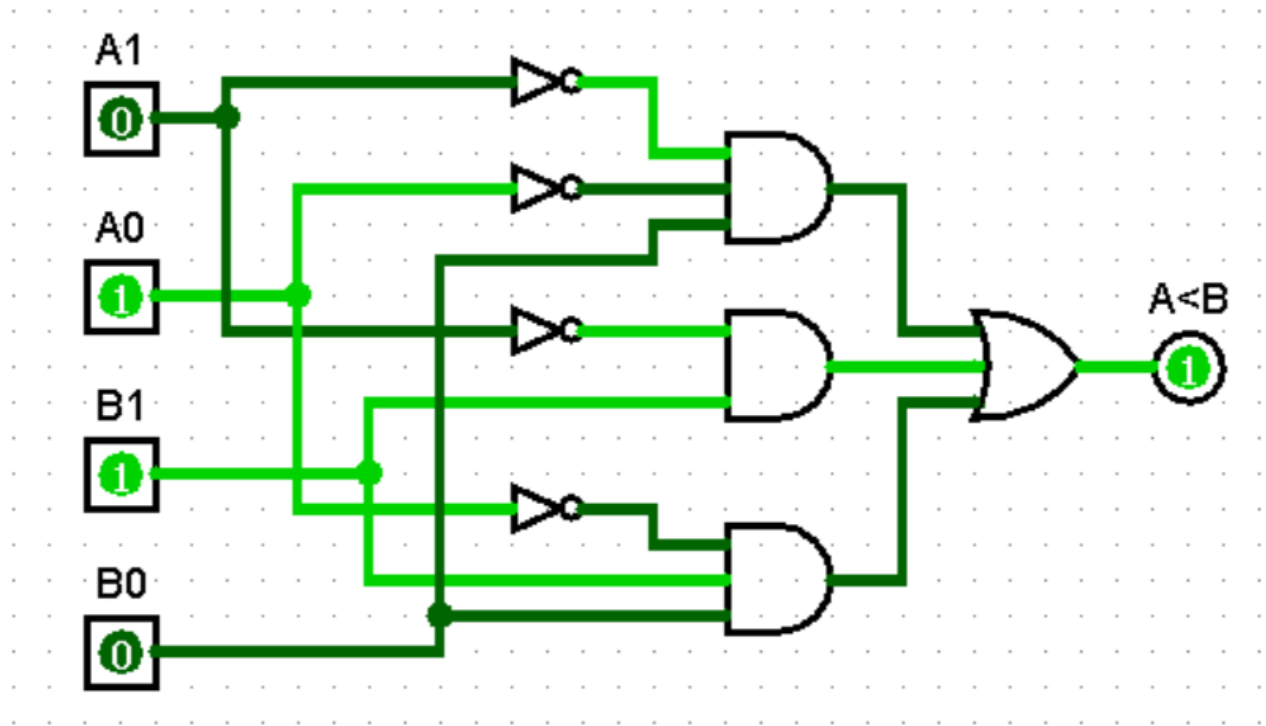

Rubric wise marks obtained:


Rubrics	Regularity		Problem Understanding & Implementation of Solution in Simulator		Testing of the Solution		Documentation		Mock Viva Test		Total out of 10
	Good (2)	Avg. (1)	Good (2)	Avg. (1)	Good (2)	Avg. (1)	Good (2)	Avg. (1)	Good (2)	Avg. (1)	

Faculty Signature

Practical 12

AIM: To implement 3 X 8 decoder in Logisim Simulator

Theory:

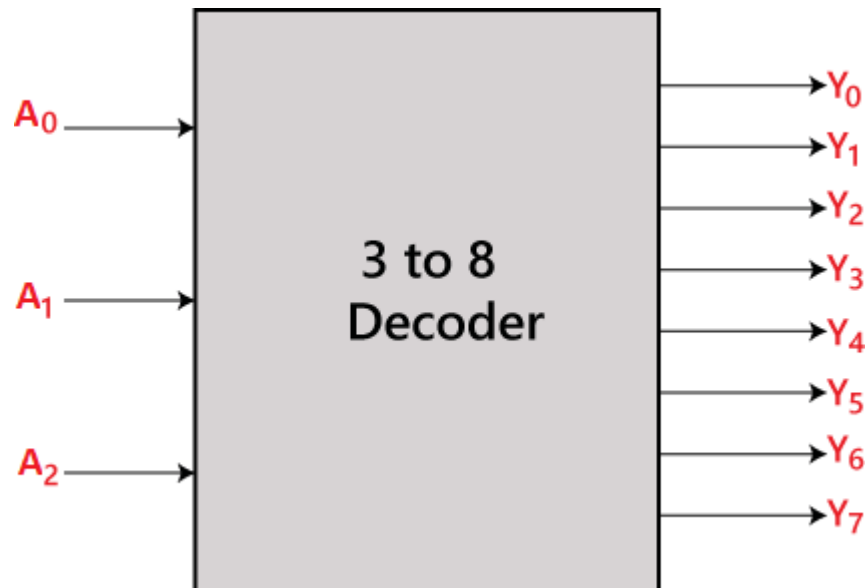

A0	A1	A2	Y0	Y1	Y2	Y3	Y4	Y5	Y6	Y7
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

$$Y_0 = A_0' A_1' A_2'$$

$$Y_1 = A_0' A_1' A_2$$

$$Y_2 = A_0' A_1 A_2'$$

$$Y_3 = A_0' A_1 A_2$$


$$Y_4 = A_0 A_1' A_2'$$

$$Y_5 = A_0 A_1' A_2$$

$$Y_6 = A_0 A_1 A_2'$$

$$Y_7 = A_0 A_1 A_2$$

Implementation:

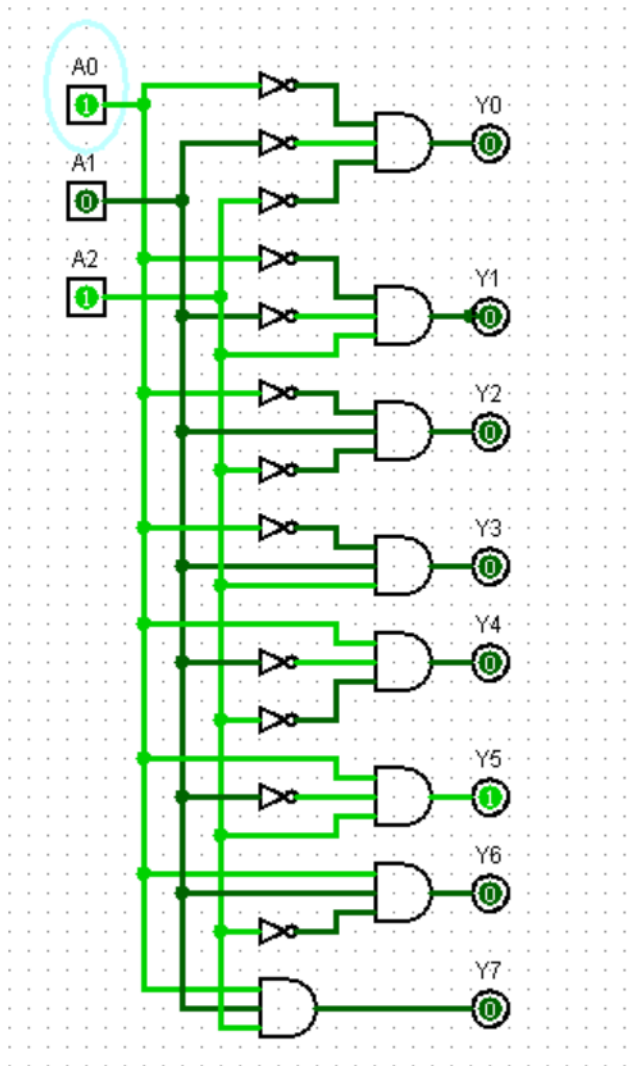

Rubric wise marks obtained:


Rubrics	Regularity		Problem Understanding & Implementation of Solution in Simulator		Testing of the Solution		Documentation		Mock Viva Test		Total out of 10
	Good (2)	Avg. (1)	Good (2)	Avg. (1)	Good (2)	Avg. (1)	Good (2)	Avg. (1)	Good (2)	Avg. (1)	

Faculty Signature


Practical 13

AIM: To implement 4 X 16 decoder with the help of 3 X 8 decoder

Theory:

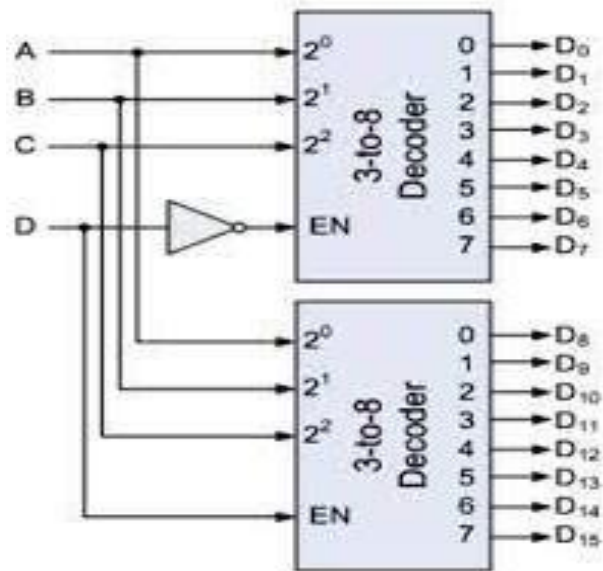

Implementation:

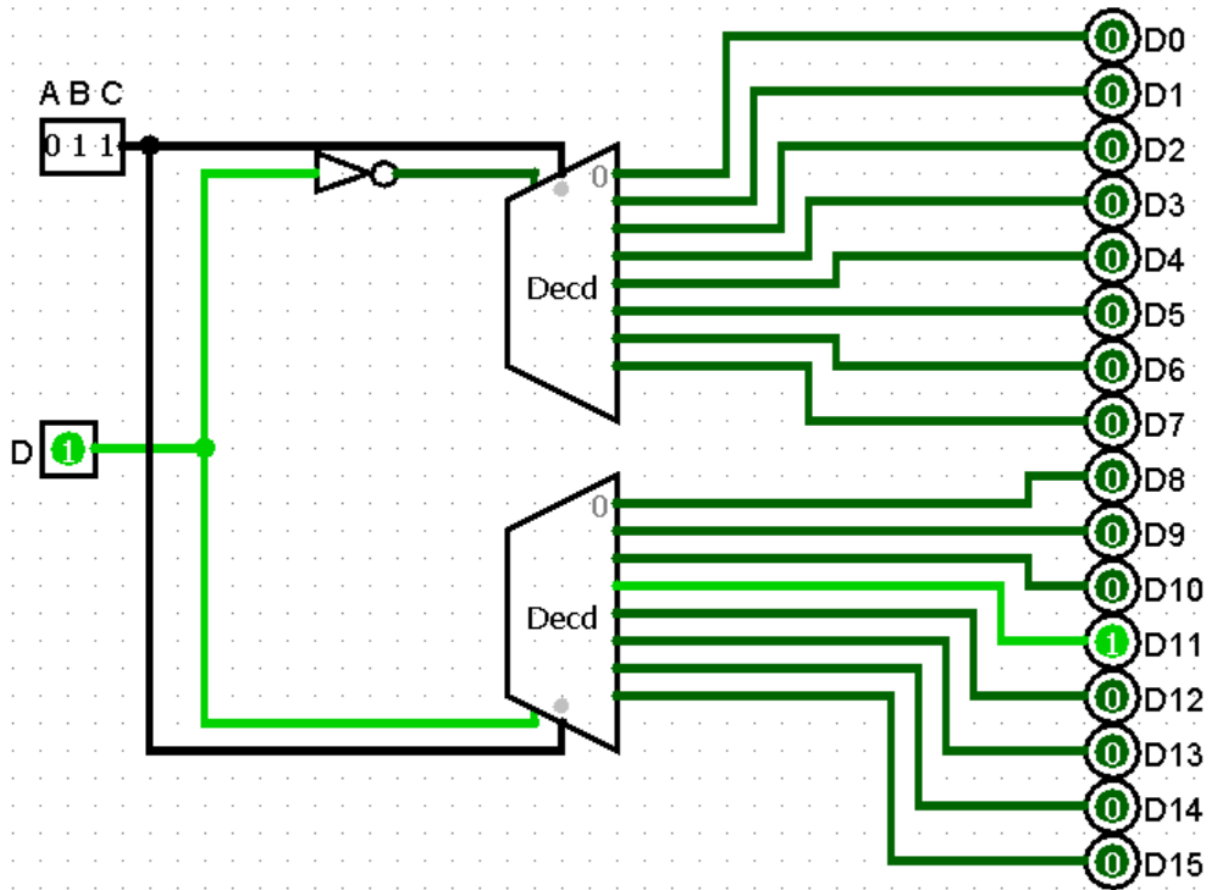

Rubric wise marks obtained:

Rubrics	Regularity		Problem Understanding & Implementation of Solution in Simulator		Testing of the Solution		Documentation		Mock Viva Test		Total out of 10
	Good (2)	Avg. (1)	Good (2)	Avg. (1)	Good (2)	Avg. (1)	Good (2)	Avg. (1)	Good (2)	Avg. (1)	

Faculty Signature

Enrolment No: - 230170116023

Page No 46


Practical 14

AIM: Draw Combinational circuit diagram for Full Adder and Full Subtractor using decoder

- FULL ADDER USING 3X8 DECODER

Inputs			Outputs	
A	B	C _{in}	Sum	Carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1


Implementation:

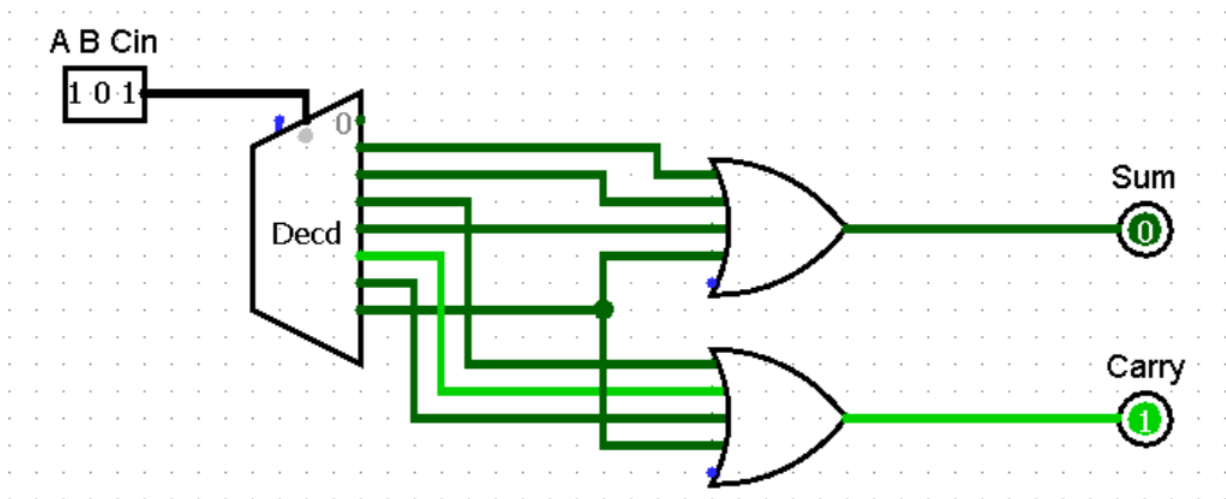

- FULL SUBTRACTOR USING 3X8 DECODER

Inputs			Outputs	
A	B	Borrow _{in}	Diff	Borrow
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

Implementation

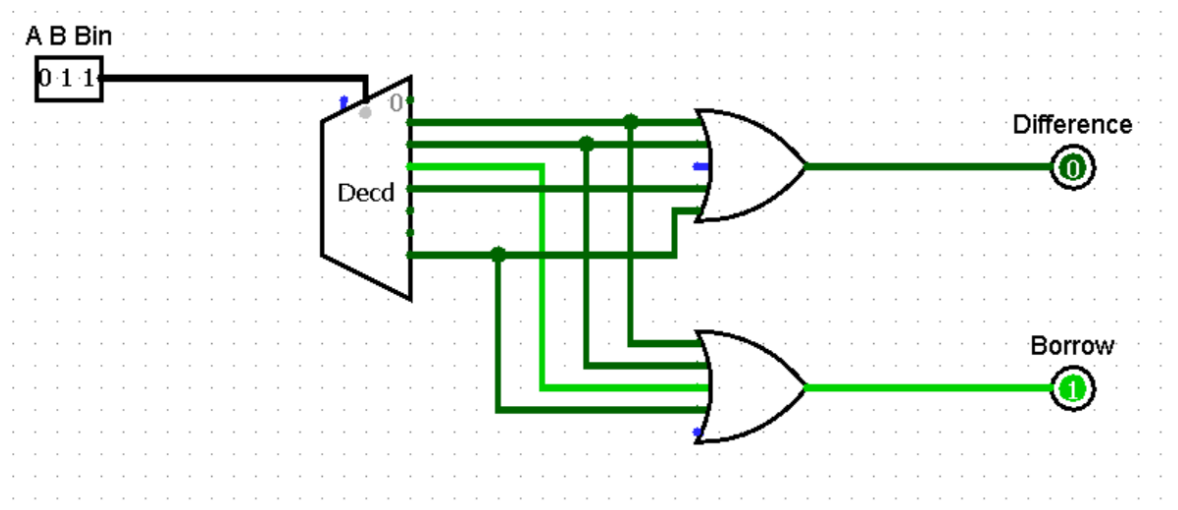

Rubric wise marks obtained:

Rubrics	Regularity		Problem Understanding & Implementation of Solution in Simulator		Testing of the Solution		Documentation		Mock Viva Test		Total out of 10
	Good (2)	Avg. (1)	Good (2)	Avg. (1)	Good (2)	Avg. (1)	Good (2)	Avg. (1)	Good (2)	Avg. (1)	

Faculty Signature

Enrolment No: - 230170116023

Page No 48

Practical 15


AIM: To implement 8 X 1 Multiplexer in Logisim Simulator

Theory:

INPUTS			Output
S ₂	S ₁	S ₀	Y
0	0	0	A ₀
0	0	1	A ₁
0	1	0	A ₂
0	1	1	A ₃
1	0	0	A ₄
1	0	1	A ₅
1	1	0	A ₆
1	1	1	A ₇

$$Y = S_2' S_1' S_0' I_0 + S_2' S_1' S_0 I_1 + S_2' S_1 S_0' I_2 + S_2' S_1 S_0 I_3 + \\ S_2 S_1' S_0' I_4 + S_2 S_1' S_0 I_5 + S_2 S_1 S_0' I_6 + S_2 S_1 S_0 I_7$$

Implementation :

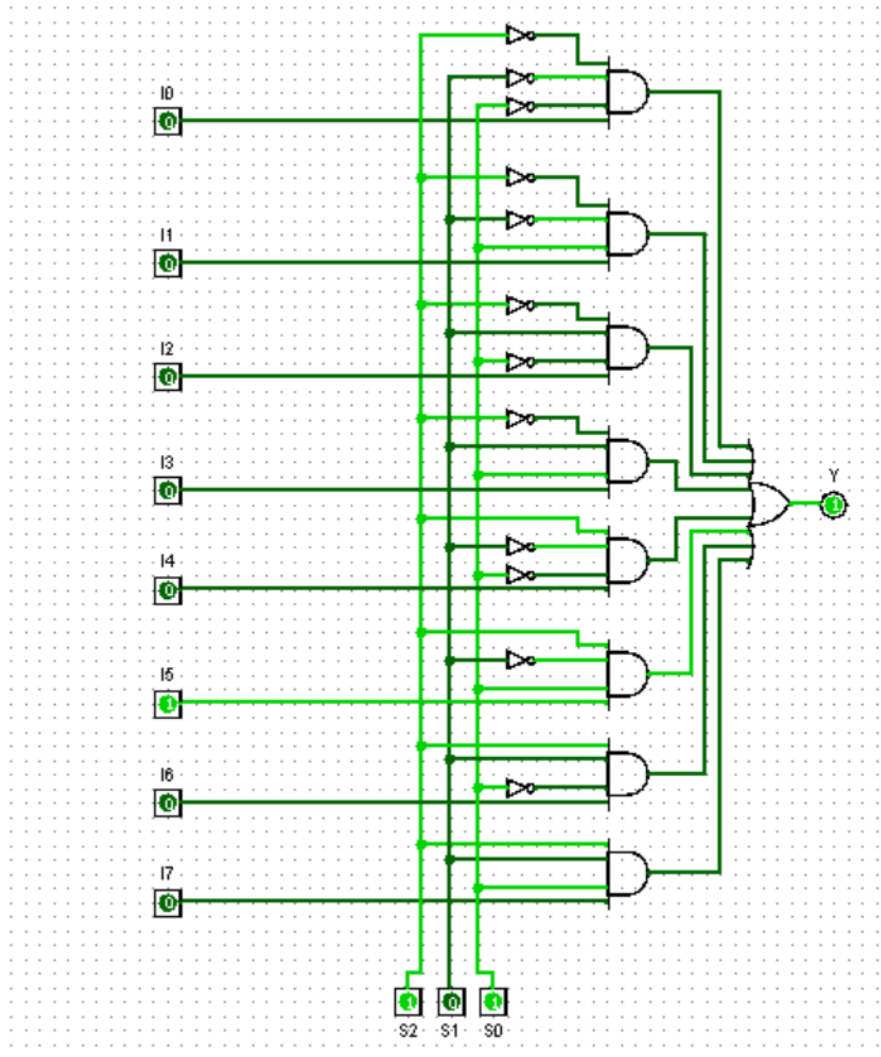

Rubric wise marks obtained:

Rubrics	Regularity		Problem Understanding & Implementation of Solution in Simulator		Testing of the Solution		Documentation		Mock Viva Test		Total out of 10
	Good (2)	Avg. (1)	Good (2)	Avg. (1)	Good (2)	Avg. (1)	Good (2)	Avg. (1)	Good (2)	Avg. (1)	

Faculty Signature

Enrolment No: - 230170116023

Page No 50